

Hardware - Tutorial 2 - Correction

Boolean Algebra and Karnaugh Maps

Exercise 1: Boolean Algebra

1) Simplify the following expressions:

- $S_1 = (A + B) \cdot (\bar{A} + \bar{B})$
- $S_2 = A \cdot B + \bar{A} \cdot \bar{B} + \bar{A} \cdot B$
- $S_3 = (A + \bar{B}) \cdot (A + B) + C \cdot (\bar{A} + B)$
- $S_4 = (A + C + D) \cdot (B + C + D)$
- $S_5 = (A \cdot \bar{B} + A \cdot B + A \cdot C) \cdot (\bar{A} \cdot \bar{B} + A \cdot B + A \cdot \bar{C})$
- $S_6 = (A + \bar{B} + C) \cdot (A + \bar{C}) \cdot (\bar{A} + \bar{B})$
- $S_7 = A \cdot B \cdot C + A \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot B \cdot \bar{C} + \bar{A} \cdot B \cdot C$
- $S_8 = A \cdot B \cdot C + A \cdot \bar{B} \cdot C + A \cdot B \cdot \bar{C} \cdot D$

Solutions:

$$\begin{aligned}
 S_1 &= (A + B) \cdot (\bar{A} + \bar{B}) \\
 S_1 &= A \cdot \bar{A} + A \cdot \bar{B} + \bar{A} \cdot B + B \cdot \bar{B} \\
 S_1 &= \cancel{A \cdot \bar{A}} + A \cdot \bar{B} + \bar{A} \cdot B + \cancel{B \cdot \bar{B}} \\
 S_1 &= A \cdot \bar{B} + \bar{A} \cdot B \\
 \boxed{S_1} &= A \oplus B
 \end{aligned}$$

$$\begin{aligned}
 S_5 &= (A \cdot \bar{B} + A \cdot B + A \cdot C) \cdot (\bar{A} \cdot \bar{B} + A \cdot B + A \cdot \bar{C}) \\
 S_5 &= (A \cdot (\bar{B} + B) + A \cdot C) \cdot (\bar{A} \cdot \bar{B} + A \cdot B + A \cdot \bar{C}) \\
 S_5 &= A \cdot (\bar{A} \cdot \bar{B} + A \cdot B + A \cdot \bar{C}) \\
 S_5 &= \cancel{A \cdot \bar{A} \cdot \bar{B}} + \cancel{A \cdot A \cdot B} + \cancel{A \cdot A \cdot \bar{C}} \\
 \boxed{S_5} &= A \cdot B + A \cdot \bar{C}
 \end{aligned}$$

$$\begin{aligned}
 S_2 &= A \cdot B + \bar{A} \cdot \bar{B} + \bar{A} \cdot B \\
 S_2 &= A \cdot B + \bar{A} \cdot (B + \bar{B}) \\
 S_2 &= A \cdot B + \bar{A} \cdot 1 \\
 S_2 &= A \cdot B + \bar{A} \\
 \boxed{S_2} &= B + \bar{A}
 \end{aligned}$$

$$\begin{aligned}
 S_6 &= (A + \bar{B} + C) \cdot (A + \bar{C}) \cdot (\bar{A} + \bar{B}) \\
 S_6 &= (A \cdot \cancel{A} + A \cdot \bar{C} + A \cdot \bar{B} + \bar{B} \cdot \bar{C} + \cancel{A \cdot C} + \cancel{C \cdot C}) \cdot (\bar{A} + \bar{B}) \\
 S_6 &= (A + \bar{B} \cdot \bar{C}) \cdot (\bar{A} + \bar{B}) \\
 S_6 &= \cancel{A \cdot \bar{A}} + A \cdot \bar{B} + \bar{A} \cdot \bar{B} \cdot \bar{C} + \bar{B} \cdot \bar{B} \cdot \bar{C} \\
 S_6 &= A \cdot \bar{B} + \bar{A} \cdot \bar{B} \cdot \bar{C} + \bar{B} \cdot \bar{C} \\
 \boxed{S_6} &= A \cdot \bar{B} + \bar{B} \cdot \bar{C}
 \end{aligned}$$

$$\begin{aligned}
 S_3 &= (A + \bar{B}) \cdot (A + B) + C \cdot (\bar{A} + B) \\
 S_3 &= A \cdot \cancel{A} + A \cdot B + A \cdot \bar{B} + \cancel{B \cdot \bar{B}} + \bar{A} \cdot C + B \cdot C \\
 S_3 &= A + A \cdot \bar{B} + A \cdot \bar{B} + \bar{A} \cdot C + B \cdot C \\
 S_3 &= A + \bar{A} \cdot C + B \cdot C \\
 S_3 &= A + C + \cancel{B \cdot C} \\
 \boxed{S_3} &= A + C
 \end{aligned}$$

$$\begin{aligned}
 S_7 &= A \cdot B \cdot C + A \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot B \cdot \bar{C} + \bar{A} \cdot B \cdot C \\
 S_7 &= B \cdot (A \cdot C + \bar{A} \cdot \bar{C} + \bar{A} \cdot C) + A \cdot \bar{B} \cdot \bar{C} \\
 S_7 &= B \cdot (A \cdot C + \bar{A}) + A \cdot \bar{B} \cdot \bar{C} \\
 S_7 &= B \cdot (\bar{A} + C) + A \cdot \bar{B} \cdot \bar{C} \\
 S_7 &= B \cdot (\bar{A} + C) + A \cdot \bar{B} \cdot \bar{C} \\
 S_7 &= B \cdot (\bar{A} \cdot \bar{C}) + \bar{B} \cdot (A \cdot \bar{C}) \\
 \boxed{S_7} &= B \oplus A \cdot \bar{C}
 \end{aligned}$$

$$\begin{aligned}
 S_4 &= (A + C + D) \cdot (B + C + D) \\
 S_4 &= A \cdot B + A \cdot C + A \cdot D + B \cdot C + C \cdot \cancel{C} + C \cdot D + B \cdot D + \cancel{C \cdot D} + D \cdot \cancel{D} \\
 S_4 &= A \cdot B + \cancel{A \cdot C} + \cancel{A \cdot D} + B \cdot C + C + \cancel{C \cdot D} + \cancel{B \cdot D} + D \\
 \boxed{S_4} &= A \cdot B + C + D
 \end{aligned}$$

$$\begin{aligned}
 S_8 &= A \cdot B \cdot C + A \cdot \bar{B} \cdot C + A \cdot B \cdot \bar{C} \cdot D \\
 S_8 &= A \cdot C \cdot (\bar{B} + B) + A \cdot B \cdot \bar{C} \cdot D \\
 S_8 &= A \cdot C + A \cdot B \cdot \bar{C} \cdot D \\
 S_8 &= A \cdot (C + B \cdot \bar{C} \cdot D) \\
 S_8 &= A \cdot (C + B \cdot D) \\
 \boxed{S_8} &= A \cdot C + A \cdot B \cdot D
 \end{aligned}$$

2) Calculate and simplify the complement of S1, S5 and S6.

Solutions:

$$\overline{S_1} = \overline{A \cdot \bar{B} + \bar{A} \cdot B}$$

$$\overline{S_1} = A \cdot \bar{B} \cdot \bar{A} \cdot B$$

$$\overline{S_1} = (\bar{A} + B) \cdot (A + \bar{B})$$

$$\overline{S_1} = A \cdot \bar{B} + A \cdot B$$

$$\boxed{\overline{S_1} = A \oplus B = \bar{A} \oplus B = A \oplus \bar{B}}$$

$$\overline{S_5} = \overline{A \cdot B + A \cdot \bar{C}}$$

$$\overline{S_5} = A \cdot (B + \bar{C})$$

$$\overline{S_5} = \bar{A} + (B + \bar{C})$$

$$\boxed{\overline{S_5} = \bar{A} + \bar{B} \cdot C}$$

$$\overline{S_6} = \overline{A \cdot \bar{B} + \bar{B} \cdot \bar{C}}$$

$$\overline{S_6} = \bar{B} \cdot (A \cdot \bar{C})$$

$$\overline{S_6} = B + (A + \bar{C})$$

$$\boxed{\overline{S_6} = B + \bar{A} \cdot C}$$

3) Design the NOT, AND and OR gates by using only NAND gates, then only NOR gates.

Solutions:

NAND gates only:

$$\bar{A} = \overline{A \cdot A}$$

$$A \cdot B = \overline{\overline{A \cdot B}}$$

$$A \cdot B = \overline{(\overline{A \cdot B}) \cdot (\overline{A \cdot B})}$$

$$A + B = \overline{\overline{A + B}}$$

$$A + B = \overline{\bar{A} \cdot \bar{B}}$$

$$A + B = \overline{(\bar{A} \cdot \bar{A}) \cdot (\bar{B} \cdot \bar{B})}$$

NOR gates only:

$$\bar{A} = \overline{A + A}$$

$$A \cdot B = \overline{\overline{A \cdot B}}$$

$$A \cdot B = \overline{\overline{A + B}}$$

$$A \cdot B = \overline{(\overline{A + A}) + (\overline{B + B})}$$

$$A + B = \overline{\overline{A + B}}$$

$$A + B = \overline{(\overline{A + B}) + (\overline{A + B})}$$

Exercise 2: Equality

Demonstrate the following equalities:

- $\overline{A \cdot C + B \cdot \bar{C}} = \bar{A} \cdot C + \bar{B} \cdot \bar{C}$
- $(A + B) \cdot (\bar{A} + C) \cdot (B + C) = (A + B) \cdot (\bar{A} + C)$

Solution:

Let's demonstrate that $\overline{A \cdot C + B \cdot \bar{C}} = \bar{A} \cdot C + \bar{B} \cdot \bar{C}$ by changing the left part of the equation into the right part:

$$\overline{A \cdot C + B \cdot \bar{C}} = \overline{A \cdot \bar{C} \cdot B \cdot \bar{C}}$$

$$A \cdot C + B \cdot \bar{C} = (\bar{A} + \bar{C}) \cdot (\bar{B} + C)$$

$$A \cdot C + B \cdot \bar{C} = \bar{A} \cdot \bar{B} + \bar{A} \cdot C + \bar{B} \cdot \bar{C} + \cancel{C \cdot \bar{C}}$$

$$A \cdot C + B \cdot \bar{C} = \cancel{\bar{A} \cdot \bar{B} \cdot C} + \cancel{\bar{A} \cdot \bar{B} \cdot \bar{C}} + \bar{A} \cdot C + \bar{B} \cdot \bar{C}$$

$$\boxed{A \cdot C + B \cdot \bar{C} = \bar{A} \cdot C + \bar{B} \cdot \bar{C}}$$

Now let's demonstrate that $(A + B) \cdot (\bar{A} + C) \cdot (B + C) = (A + B) \cdot (\bar{A} + C)$ by developing each side of the equation:

$$(A + B) \cdot (\bar{A} + C) \cdot (B + C) = (A + B) \cdot (\bar{A} + C)$$

$$(\cancel{A \cdot \bar{A}} + A \cdot C + \bar{A} \cdot B + B \cdot C) \cdot (B + C) = \cancel{A \cdot \bar{A}} + A \cdot C + \bar{A} \cdot B + B \cdot C$$

$$A \cdot B \cdot C + A \cdot C \cdot \cancel{C} + \bar{A} \cdot B \cdot \cancel{B} + \bar{A} \cdot B \cdot C + \cancel{B \cdot B \cdot C} + B \cdot C \cdot \cancel{C} = A \cdot C + \bar{A} \cdot B + B \cdot C$$

$$\cancel{A \cdot B \cdot C} + A \cdot C + \bar{A} \cdot B + B \cdot C = A \cdot C + \bar{A} \cdot B + B \cdot C$$

$$A \cdot C + \bar{A} \cdot B + B \cdot C = A \cdot C + \bar{A} \cdot B + B \cdot C$$

Exercise 3: Problem

Given 3 binary variables A, B and C, design an expression S that is true only if the number of true variables is odd.

Solution:

In order to extract a boolean expression from a given problem, we first need to fill a truth table of that problem. Then we can extract the terms of the expression from the truth table by simply finding the expression of each line where S is true.

A	B	C	S	
0	0	0	0	
0	0	1	1	$\rightarrow \bar{A} \cdot \bar{B} \cdot C$
0	1	0	1	$\rightarrow \bar{A} \cdot B \cdot \bar{C}$
0	1	1	0	
1	0	0	1	$\rightarrow A \cdot \bar{B} \cdot \bar{C}$
1	0	1	0	
1	1	0	0	
1	1	1	1	$\rightarrow A \cdot B \cdot C$

Finally we have to compute and simplify the full expression:

$$S = \bar{A} \cdot \bar{B} \cdot C + \bar{A} \cdot B \cdot \bar{C} + A \cdot \bar{B} \cdot \bar{C} + A \cdot B \cdot C$$

$$S = \bar{A} \cdot (\bar{B} \cdot C + B \cdot \bar{C}) + A \cdot (\bar{B} \cdot \bar{C} + B \cdot C)$$

$$S = \bar{A} \cdot (B \oplus C) + A \cdot (\bar{B} \oplus \bar{C})$$

$$\boxed{S = A \oplus B \oplus C}$$

Exerice 4: 3 variables Karnaugh maps

Given a number N encoded in 3 bits binary (C, B, A) with C the most significant bit, find the most simplified boolean expression of $S = f(N)$ using Karnaugh maps for each of the following:

- $S_1 = 1$ when $N \geq 3$
- $S_2 = 1$ when $2 < N \leq 6$
- $S_3 = 1$ when $N = 1, 3, 5$
- $S_4 = 1$ when $N = 1, 3, 5$ and S is undefined when $N = 0$ or 7

Solution:

To solve theses problems, we will first fill a truth table for each S , then fill and solve some Karnaugh Maps and finally extract the expressions from the Karnaugh Maps:

C	B	A	S_1	S_2	S_3	S_4
0	0	0	0	0	0	\emptyset
0	0	1	0	0	1	1
0	1	0	0	0	0	0
0	1	1	1	1	1	1
1	0	0	1	1	0	0
1	0	1	1	1	1	1
1	1	0	1	1	0	0
1	1	1	1	0	0	\emptyset

S_1		BA			
		00	01	11	10
C	0	0	0	1	0
	1	1	1	1	1

S_2		BA			
		00	01	11	10
C	0	0	0	1	0
	1	1	1	0	1

S_3		BA			
		00	01	11	10
C	0	0	1	1	0
	1	0	1	0	0

S_4		BA			
		00	01	11	10
C	0	\emptyset	1	1	0
	1	0	1	\emptyset	0

$$S_1 = B \cdot A + C$$

$$S_2 = \bar{C} \cdot B \cdot A + C \cdot \bar{B} + C \cdot \bar{A}$$

$$S_3 = \bar{C} \cdot A + \bar{B} \cdot A$$

$$S_4 = A$$

$$S_2 = \bar{C} \cdot (B \cdot A) + C \cdot (\bar{B} + \bar{A})$$

$$S_2 = \bar{C} \cdot (B \cdot A) + C \cdot \overline{(B \cdot A)}$$

$$S_2 = C \oplus B \cdot A$$

Exercise 5: Problem

We want to design a circuit that can perform the two's complement of a 3 bits binary number. This circuit has 3 inputs (C, B, A) and 3 outputs (C', B', A') with C and C' their most significant bits.

1) Write down the truth table of each of these outputs.

Solution:

C	B	A	C'	B'	A'
0	0	0	0	0	0
0	0	1	1	1	1
0	1	0	1	1	0
0	1	1	1	0	1
1	0	0	1	0	0
1	0	1	0	1	1
1	1	0	0	1	0
1	1	1	0	0	1

2) Find their most simplified expression using Karnaugh maps.

Solution:

C'		BA			
		00	01	11	10
C	0	0	1	1	1
	1	1	0	0	0

B'		BA			
		00	01	11	10
C	0	0	1	0	1
	1	0	1	0	1

A'		BA			
		00	01	11	10
C	0	0	1	1	0
	1	0	1	1	0

$$C' = C \cdot \bar{B} \cdot \bar{A} + \bar{C} \cdot A + \bar{C} \cdot B$$

$$B' = \bar{B} \cdot A + B \cdot \bar{A}$$

$$A' = A$$

$$C' = C \cdot (\bar{B} \cdot \bar{A}) + \bar{C} \cdot (B + A)$$

$$B' = B \oplus A$$

$$C' = C \cdot \overline{(B + A)} + \bar{C} \cdot (B + A)$$

$$C' = C \oplus (B + A)$$

Exercise 6: 4 variables Karnaugh maps

Given a number N encoded in 4 bits binary (D, C, B, A) with D the most significant bit, find the most simplified boolean expression of $S = f(N)$ using Karnaugh maps for each of the following:

- $S_1 = 1$ when $N \geq 10$
- $S_2 = 1$ when $N = 0, 4, 8, 10, 12$ or 14
- $S_3 = 1$ when $N = 0, 2, 5, 7, 8, 10, 13$ or 15
- $S_4 = 1$ when $N = 2, 10, 11$ or 14
- $S_5 = 1$ when $N = 2, 10, 11$ or 14 and S is undefined when $N = 6, 9, 13$ or 15

Solution:

Let's fill directly the Karnaugh Maps for each expression:

S_1		BA			
		00	01	11	10
DC	00	0	0	0	0
	01	0	0	0	0
	11	1	1	1	1
	10	0	0	1	1

S_2		BA			
		00	01	11	10
DC	00	1	0	0	0
	01	1	0	0	0
	11	1	0	0	1
	10	1	0	0	1

S_3		BA			
		00	01	11	10
DC	00	1	0	0	1
	01	0	1	1	0
	11	0	1	1	0
	10	1	0	0	1

S_4		BA			
		00	01	11	10
DC	00	0	0	0	1
	01	0	0	0	0
	11	0	0	0	1
	10	0	0	1	1

S_5		BA			
		00	01	11	10
DC	00	0	0	0	1
	01	0	0	0	0
	11	0	0	0	1
	10	0	0	1	1

Then we can extract the boolean expression of each of the maps:

$$S_1 = D \cdot C + D \cdot B$$

$$S_2 = \bar{B} \cdot \bar{A} + D \cdot \bar{A}$$

$$S_3 = \bar{C} \cdot \bar{A} + C \cdot A$$

$$S_4 = D \cdot B \cdot \bar{A} + \bar{C} \cdot B \cdot \bar{A} + D \cdot \bar{C} \cdot B$$

$$S_5 = D \cdot A + B \cdot \bar{A}$$

$$S_3 = \overline{C \oplus A}$$