

Hardware - Tutorial 2

Boolean Algebra and Karnaugh Maps

Exercise 1: Boolean Algebra

1) Simplify the following expressions:

- $S_1 = (A + B) \cdot (\bar{A} + \bar{B})$
- $S_2 = A \cdot B + \bar{A} \cdot \bar{B} + \bar{A} \cdot B$
- $S_3 = (A + \bar{B}) \cdot (A + B) + C \cdot (\bar{A} + B)$
- $S_4 = (A + C + D) \cdot (B + C + D)$
- $S_5 = (A \cdot \bar{B} + A \cdot B + A \cdot C) \cdot (\bar{A} \cdot \bar{B} + A \cdot B + A \cdot \bar{C})$
- $S_6 = (A + \bar{B} + C) \cdot (A + \bar{C}) \cdot (\bar{A} + \bar{B})$
- $S_7 = A \cdot B \cdot C + A \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot B \cdot \bar{C} + \bar{A} \cdot B \cdot C$
- $S_8 = A \cdot B \cdot C + A \cdot \bar{B} \cdot C + A \cdot B \cdot \bar{C} \cdot D$

2) Calculate and simplify the complement of S1, S5 and S6.

3) Design the NOT, AND and OR gates by using only NAND gates, then only NOR gates.

Exercise 2: Equality

Demonstrate the following equalities:

- $\overline{A \cdot C + B \cdot \bar{C}} = \bar{A} \cdot C + \bar{B} \cdot \bar{C}$
- $(A + B) \cdot (\bar{A} + C) \cdot (B + C) = (A + B) \cdot (\bar{A} + C)$

Exercise 3: Problem

Given 3 binary variables A, B and C, design an expression S that is true only if the number of true variables is odd.

Exercise 4: 3 variables Karnaugh maps

Given a number N encoded in 3 bits binary (C, B, A) with C the most significant bit, find the most simplified boolean expression of $S = f(N)$ using Karnaugh maps for each of the following:

- $S_1 = 1$ when $N \geq 3$
- $S_2 = 1$ when $2 < N \leq 6$
- $S_3 = 1$ when $N = 1, 3, 5$
- $S_4 = 1$ when $N = 1, 3, 5$ and S is undefined when $N = 0$ or 7

Exercise 5: Problem

We want to design a circuit that can perform the two's complement of a 3 bits binary number.

This circuit has 3 inputs (C, B, A) and 3 outputs (C', B', A') with C and C' their most significant bits.

- 1) Write down the truth table of each of these outputs.
- 2) Find their most simplified expression using Karnaugh maps.

Exercise 6: 4 variables Karnaugh maps

Given a number N encoded in 4 bits binary (D, C, B, A) with D the most significant bit, find the most simplified boolean expression of $S = f(N)$ using Karnaugh maps for each of the following:

- $S = 1$ when $N \geq 10$
- $S = 1$ when $N = 0, 4, 8, 10, 12$ or 14
- $S = 1$ when $N = 0, 2, 5, 7, 8, 10, 13$ or 15
- $S = 1$ when $N = 2, 10, 11$ or 14
- $S = 1$ when $N = 2, 10, 11$ or 14 and S is undefined when $N = 6, 9, 13$ or 15